

- 1) Explain V-I characteristics of LCD?
- 2) Draw the circuit diagram of an NPN junction transistor in CE Configuration and describe the static input and output characteristics. Also define active, saturation and cut-off regions and saturation resistance of a CE transistor.
- 3) Explain about input and output characteristics of a transistor when it is connected in Common base Configuration.

1) V-I characteristics of LCD :-

some characteristics of liquid crystal displays

(LCDs)

Brightness :- LCDs offer excellent brightness which contributes to their crystal clear picture quality.


Contrast :- LCDs have superior contrast, which also contributes to their crystal clear picture quality.

Resolution :- LCDs provide excellent resolution & display information best at their native resolution.

Sharpness :- LCDs provide perfect sharpness at their native resolution.

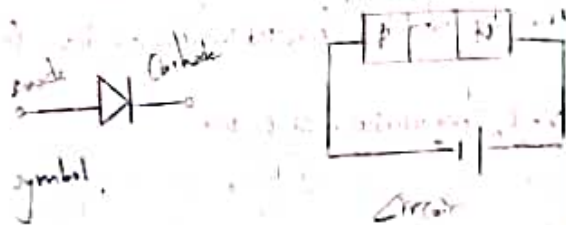1) LCD [liquid crystal display] is a type of flat panel display, which makes use of liquid crystal in its primary form of operation.

A liquid-crystal display (LCD) is a flat-panel display or other electronically modulated optical device that uses the light-modulating properties of liquid crystals. Combined with polarizers, liquid crystals do not emit light directly but instead use a back light or reflector to produce image in color or monochrome.



### Construction of LED diode circuit diagram

A liquid crystal display [LCD] is made of two layers, each containing two polarized filters and electrodes, the layers are made of combination of liquid and solid materials, with solid compound being a crystal the liquid crystal. Used in LCD can have different chemical formula.

### How circuit work


An external light source passes through one of the polarized glasses.

An electric current is applied to the liquid or the liquid crystal molecule, causing them to align the polarized light travels from the first layer to the second polarized glass, creating an image on the screen.
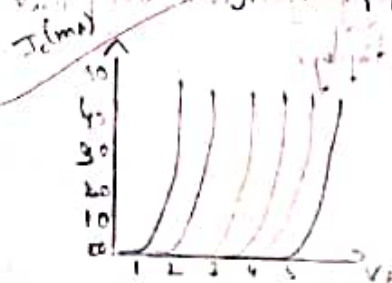
### Working principle of LED diode

The principle behind the LCD is that when an electric current is applied to the liquid crystal molecules, the molecules tend to untwist this causes the angle of the polarized light which is passing through the molecules of the polarized glass and also causes a change in the angle of the top polarizing filter.

The basic principle of LED is that liquid crystal (LC) molecules work at light value to control the light. The LC-molecules is usually a rod-like (or) disk-like shape and can rotate under an electric field. LCD displays work by controlling the liquid crystal to either block or allow light to pass through, creating characteristics and symbols on the screen. It is controlled by sending data and commands to its controller, which is then manages the display of information.



V-I characteristics of LED diode



LCD displays are not only small in size, thin in thickness, light in weight, low energy consumption, low in operating voltage (1.5 to 6V) and non-radiative. Screens free and can be directly method.

It is lighter than and flexible LED provides excellent resolution, brightness and contrast so the picture quality is clearly. Clear LCDs can be suitable with CMOS integrated circuits so making an LCD is very easy it gives perfect sharpness and better resolution.

LCD monitors radiate much less than CRT monitors. Low not completely without radiation and electronic products have more or less radiation which is a harm for those who work in front of computers all day long.

### Applications :-

LCDs are used in a wide range of applications including LCD television, Computer monitor, Instrument panels, Car radars, Cockpit displays, and indoor and outdoor signage.


clocks used in displaying digital wall clocks portable gaming device and car displays.

### 2A] Common emitter Configuration :- 23AM1A0417


The Configuration in which emitter is connected to the collector and base is known as a Common emitter Configuration.

This arrangement places the emitter between the collector and the base. The emitter and base forms the connection for the input circuit, while the collector and emitter provides the connection for the output circuit.

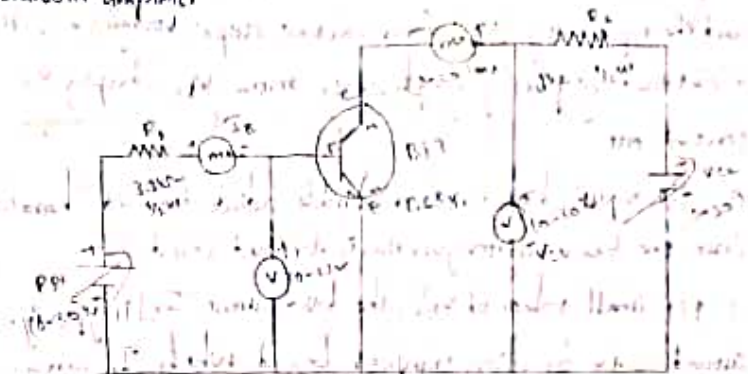→ The Common emitter circuit is the most widely used of junction transistor amplifiers.



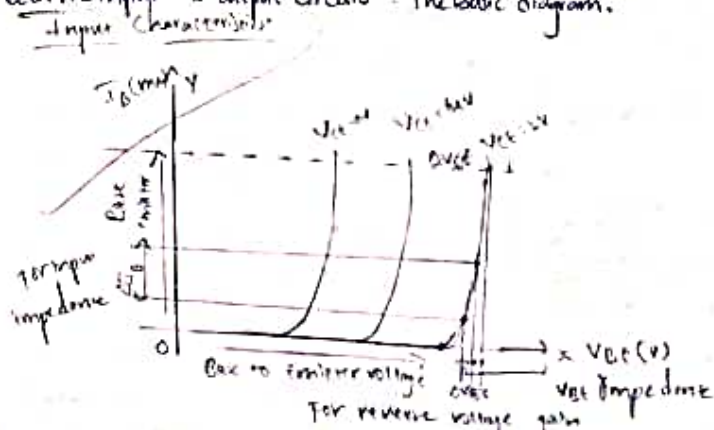In the Common emitter (CE) Configuration the emitter is common to both the input and output circuits. The basic diagram.



NPN transistor :- The transistor has three terminal emitter (E)

Base (B) Collector (C)

Input side :- The input signal is applied b/w the base (B) and emitter (E)

Resistor :- A resistor is connected in series with the base terminal to limit the base current.

Input characteristics :- The relationship b/w the input current and the input voltage ( $V_{BE}$ ) for a constant output voltage ( $V_{CE}$ ). It is obtained by plotting a graph of  $I_B$  versus  $V_{BE}$ , keeping  $V_{CE}$  constant.

→ The input characteristic resembles a diode forward characteristic since the base-emitter junction is forward biased.

→ For small values of  $V_{BE}$ , the base current ( $I_B$ ) is typically around 0.7V for silicon transistor beyond which  $I_B$  increases rapidly.

Output characteristics



Output side

Collector :- The output signal ( $V_{out}$ ) is taken across the collector (C) and emitter (E)

Resistor :- A load resistor is connected in series with the collector terminal.

$V_{CC}$  :- The supply voltage ( $V_{CC}$ ) is connected to the collector

Output characteristics

The relationship b/w the output current ( $I_C$ ) and the output voltage ( $V_{CE}$ ) for a constant input current ( $I_B$ ). It is obtained by plotting a graph of  $I_C$  versus  $V_{CE}$ , keeping  $I_B$  constant.

→ The output characteristics show three distinct regions: the active region, the saturation region, and cutoff region.

→ In the active region,  $I_C$  depends on  $I_B$  and is relatively independent of  $V_{CE}$ .

→ In the saturation region, both the base-collector and base-emitter junctions are forward biased, resulting in maximum  $I_C$ .

→ In the cutoff region, both junctions are reverse biased, and  $I_C$  is minimal (close to zero).

Active region :- In this region the transistor operates as an amplifier; the base-emitter junction is forward biased, and the base-collector junction is reverse biased. The collector current ( $I_C$ ) is proportional to the base current ( $I_B$ ) and the transistor operates in a linear region.



Saturation region :- In this region both the base-emitter and base-collector junctions are forward biased the transistor is fully on, and behaves like a closed switch and the Collector-emitter voltage is very low.

Cutoff region :- In this region both the base-emitter and base-collector junctions are reverse biased the transistor is fully off, and the collector current ( $I_c$ ) is minimum close to zero, the transistor behaves like an open switch.

Saturation resistance :- The saturation resistance of a C.P. transistor refers to the small present b/w the Collector and emitter terminals when the transistor is in the saturation region.


The characteristics and regions are critical in understanding the operation of the transistor in various applications, particularly in amplification and switching.

### 3A] :- Common base Configuration :-

Common base Configuration also known as grounded base Configuration, is a circuit arrangement for a bipolar junction transistor (BJT) where the base terminal is shared by both the input and output circuits. In this Configuration, the input signal is applied to the emitter terminal, and the output is taken from the Collector terminal.

→ Input and output terminals the i/p terminal is emitter base (E-B) and the output terminal is Collector-base (C-B)

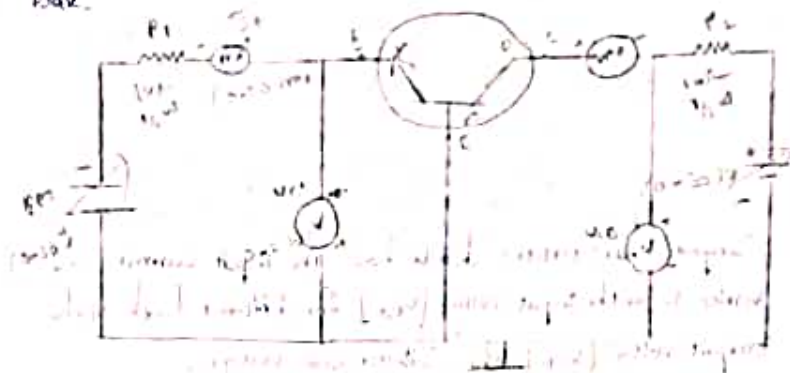→ CB Configuration can be used as an amplifier. In this circuit arrangement base, and output is taken from the Collector and base.



In Common base Configuration, the transistor input and output characteristics can be analyzed.

#### Input characteristics :-


\* Input terminal :- emitter (E) with respect to base (B) which is typically grounded.

\* Input voltage :- ( $V_{BE}$ ) voltage b/w the emitter and base

\* Input Current ( $I_{BE}$ ) :- Current flowing into the emitter

The input current increases rapidly with small increase in the emitter-base voltage ( $V_{BE}$ ) after surpassing the cut-in voltage.

## Input characteristics

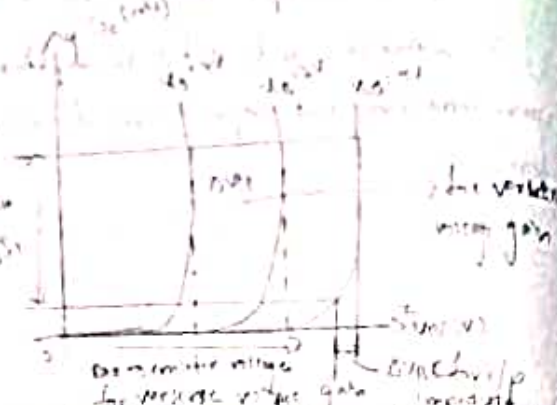

Input characteristics describe how the input current ( $I_E$ ) varies with the input voltage ( $V_{BE}$ ) for different levels of the output voltage ( $V_{CE}$ ), the collector base voltage.

Typically, the input characteristics resemble the forward-biased diode curve as the emitter base junction is forward-biased.

Input impedance :- low because, the emitter base junction is forward biased.

Output characteristics :-

output terminal :- collector with respect to the base.

output voltage :-  $V_{CE}$  :- voltage b/w the collector and base.

output current ( $I_C$ ) :- Into current flowing into the collector

The output characteristics describe how the output current ( $I_C$ ) varies with the output voltage ( $V_{CE}$ ) for different levels of input current ( $I_E$ ).



for a constant input current ( $I_E$ ) the output current ( $I_C$ ) remains nearly constant over a wide range of collector-base voltage ( $V_{CE}$ ). This is the active region, where the transistor operates efficiently as an amplifier. In this region  $I_C \approx I_E$ , since the common base current gain ( $\alpha$ ) is close to 1.

output impedance :-

High because the collector base junction is reverse biased in the active region.

Current gain :- less than 1 ( $\alpha \approx 0.95$  to  $0.99$ ) because in a common base configuration the current gain is the ratio of the collector current ( $I_C$ ) to the emitter current ( $I_E$ ).

The common base configuration is typically used in high-frequency applications due to its stability and low input impedance.